

Assinment-3
ANSWER KEY

1. (c) Here the system can be considered as two capacitors C_1 and C_2 connected in series.

CASE BASED STUDY QUESTION

2. 1.(c) 2. (b) 3. (b) 4.(c)

2 MARKS ANSWERS


3. The capacitance of the parallel plate capacitor, filled with dielectric medium of dielectric constant K is given by $C=K \epsilon_0 A/d$

The capacitance of the parallel plate capacitor decreases with the removal of dielectric medium as for air or vacuum $K = 1$ and for dielectric $K > 1$.

If we disconnect the battery from capacitor, then the charge stored will remain the same due to conservation of charge.

The potential difference across the plates of the capacitor is given by $V =q/C$
Since q is constant and C decreases which in turn increases V and therefore E increases as $E = V/d$.

4.

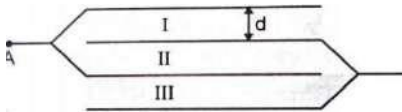

$$C_p=3C =3 A\epsilon_0/d$$

5. The capacitance of this capacitor is 221.2×10^{-13} F. The charge stored in any one of the plates 221.2 pC.

3 MARKS ANSWERS

6. Dielectric slab of thickness 5mm is equivalent to an air capacitor of thickness = $\frac{5}{10}$ mm

Effective separation between the plates with air in between is = 5.5 mm

$$\text{Effective new capacitance} = 200 \mu\text{F} \times \frac{5}{5.5} = 182 \mu\text{F}$$

$$\text{(i) Effective new electric field} = \frac{100}{5.5 \times 10^{-3}} = 18182 \text{ V/m}$$

$$\text{New energy stored / original energy stored} = 10/11$$

7. Given : $C_A= C_B = C$, Dielectric constant = K

$$\text{Energy stored} = \frac{1}{2} C v^2 \quad \text{(i)}$$

$$\text{Net capacitance with switch S closed} = C+C= 2C$$

$$E_1= \text{Energy stored} = CV^2 \quad \text{(ii)}$$

After switch S is opened, capacitance of each capacitor = KC

$$\text{Energy stored in capacitor A} = \frac{1}{2} kcv^2 \quad (\text{iii})$$

For capacitor B,

$$\text{Energy stored} = \frac{cv^2}{2k} \quad (\text{iv})$$

From equations (iii) & (iv)

$$E = \text{Total energy stored} = \frac{1}{2} cv^2 \left(\frac{k^2+1}{k} \right)$$

$$\text{Required Ratio} = \frac{E_1}{E_2} = \frac{2k}{k^2+1}$$

5-MARKS ANSWERS

8. Answer:

$$\text{Given : } q_1 = 360 \mu\text{C} = 360 \times 10^{-6} \mu\text{C}, \quad q_2 = 120 \mu\text{C} \\ = 120 \times 10^{-6} \text{ C}$$

$$C = \frac{q_1}{V_1}. \text{ Also } C = \frac{q_2}{V_2} \text{ and } C = \frac{q_3}{V_3}$$

[∵ Capacitor is the same

$$\therefore \frac{q_1}{V_1} = \frac{q_2}{V_2}$$

$$\Rightarrow \frac{(360 \times 10^{-6})}{V} = \frac{(120 \times 10^{-6})}{(V - 120)}$$

On solving, $V = 180 \text{ V}$

$$C = \frac{360 \times 10^{-6}}{180}$$

= $2 \mu\text{F}$ is the unknown capacitance.

Now the voltage has been increased by 120 V,
then $V = 180 + 120 = 300 \text{ V}$

$$C = \frac{q_3}{300} = 2 \mu\text{F}$$

$$q_3 = 300 \times \mu\text{C}$$

$q_3 = 600 \mu\text{C}$ would be charge on the capacitor if voltage were increased by 120 V.

[Ans : $V = 60 \text{ V}$, $c = 2 \text{ pF}$, $Q_3 = 200 \mu\text{C}$].

9.

Given : $q_1 = 360 \mu\text{C} = 360 \times 10^{-6} \mu\text{C}$, $q_2 = 120 \mu\text{C} = 120 \times 10^{-6} \text{C}$

$$C = \frac{q_1}{V_1} \text{ Also } C = \frac{q_2}{V_2} \text{ and } C = \frac{q_3}{V_3}$$

[\because Capacitor is the same

$$\therefore \frac{q_1}{V_1} = \frac{q_2}{V_2}$$

$$\Rightarrow \frac{(360 \times 10^{-6})}{V} = \frac{(120 \times 10^{-6})}{(V - 120)}$$

On solving, $V = 180 \text{ V}$

$$C = \frac{360 \times 10^{-6}}{180}$$

= $2 \mu\text{F}$ is the unknown capacitance.

Now the voltage has been increased by 120 V, then $V = 180 + 120 = 300 \text{ V}$

$$C = \frac{q_3}{300} = 2 \mu\text{F}$$


$$q_3 = 300 \times \mu\text{C}$$

$q_3 = 600 \mu\text{C}$ would be charge on the capacitor if voltage were increased by 120 V.

[Answer : $V = 120 \text{ V}$, $c = 2 \mu\text{F}$, $Q = 400 \mu\text{C}$]

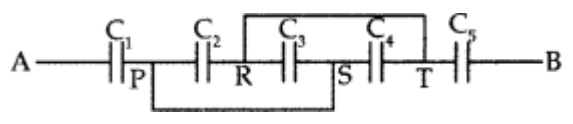10.

Given : $C_1 = C_2 = C_3 = C_4 = C_5 = 2 \mu\text{F} = 2 \times 10^{-6} \text{ F}$



(i) Capacitors C_2, C_3 and C_4 are in parallel

$$\therefore C_{234} = C_2 + C_3 + C_4 = 2 + 2 + 2$$

$$\therefore C_{234} = 6 \mu\text{F}$$

Capacitors C_1, C_{234} and C_5 are in series

$$\therefore \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{234}} + \frac{1}{C_5} = \frac{1}{2} + \frac{1}{6} + \frac{1}{2} = \frac{7}{6} \mu\text{F}$$

$$C_{equivalent} = \frac{6}{7} \mu\text{F} = \frac{6}{7} 10^{-6} \text{ F}$$

(ii) Charge drawn from the source

$$Q = C_{eq} V = \frac{6}{7} \times 7 \mu\text{C} = 6 \mu\text{C}$$